



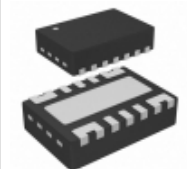
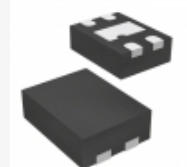



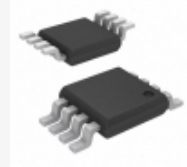


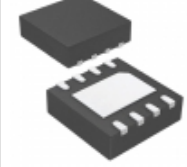











AOZ1335DI_2

| | |
|--|--|
| <div></div> | <div><div><div>Part Number: AOZ1335DI_2</div><div>Manufacturer: Alpha and Omega Semiconductor, Inc.</div><div>Description: IC SMART LOAD SW 2CH 14DFN</div><div>Data sheet:</div></div><div><div>RoHs Status: Lead free / RoHS Compliant</div><div>Ship From: Hong Kong</div><div>Shipment Way: DHL/Fedex/TNT/UPS/EMS</div></div></div> |
| <div>Images are for reference only. See Product Specifications for product details. Buy AOZ1335DI_2 with confidence from Component-World.HK, 1 Year Warranty</div> | <div>Request For Quotation</div> |

| PRODUCT PARAMETER | | | |
|--|---|--------------------------------|---|
| Part Number | AOZ1335DI_2 | Manufacturer | Alpha and Omega Semiconductor, Inc. |
| Description | IC SMART LOAD SW 2CH 14DFN | Lead Free Status / RoHS Status | Lead free / RoHS Compliant |
| Quantity Available | 4500 pcs | Data sheet | |
| Category | Integrated Circuits (ICs) | Series | * |
| Moisture Sensitivity Level (MSL) | 1 (Unlimited) | Lead Free Status / RoHS Status | Lead free / RoHS Compliant |
| <div>Component-World.com is a Reliable Stocking Distributor of Electronic Components. We specialize in all Alpha and Omega Semiconductor, Inc. series electronic components. We have 4500 pieces of Alpha and Omega Semiconductor, Inc. AOZ1335DI_2 in stock available now. Request a quote from electronics components distributor at Component-World.com, our sales team will contact you within 24 hours. RFQ Email: info@Components-World.com</div> | | | |

| RELATED PRODUCTS | | | |
|--|--|--|----------------|
|  | Part#: AOZ1335DI Description: IC SMART LOAD SW 2CH 14DFN | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1360AIL_2 Description: IC LOAD SW HI-SIDE CC 8SOIC | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1331DI Description: DUAL SMART LOAD SWITCH | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1321DI-03 Description: IC LOAD SW HI SIDE P-CH 4DFN | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1321DI-02 Description: IC LOAD SW HI SIDE P-CH 4DFN | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1321DI-05 Description: IC LOAD SW HI SIDE P-CH 4DFN | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1341EI Description: IC PWR DIST SW USB 2CH 8MSOP | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1341EI-1 Description: IC PWR DIST SW USB 2CH 8MSOP | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1341AI-1 Description: IC PWR DIST SW USB 2CH 8SOIC | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1342PI Description: IC PWR DIST SW USB 2CH 8SO | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1336DI Description: 4A 5.5V LOAD SWITCH | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1360AIL Description: IC LOAD SW HI-SIDE CC 8SOIC | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1321DI-04 Description: IC LOAD SW HI SIDE P-CH 4DFN | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1321DI-01 Description: IC LOAD SW HI SIDE P-CH 4DFN | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1334DI-02 Description: IC LOAD SWITCH 10A 5.5V | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1342PI-1 Description: IC PWR DIST SW USB 2CH 8SO | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1341AI Description: IC PWR DIST SW USB 2CH 8SOIC | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1334DI-01 Description: 10A 5.5V LOAD SWITCH | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1360AIL_3 Description: IC LOAD SW HI-SIDE CC 8SOIC | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |
|  | Part#: AOZ1321DI-06 Description: IC LOAD SW HI SIDE P-CH 4DFN | Manufacturers: Alpha and Omega Semiconductor, Inc. | <div>RFQ</div> |

| Related keywords for AOZ1335DI_2 | | | |
|-------------------------------------|-------------------------------------|-------------------------------------|--|
| Alpha and Omega Semiconductor, Inc. | AOZ1335DI_2 distributor | AOZ1335DI_2 supplier | AOZ1335DI_2 price |
| AOZ1335DI_2 | AOZ1335DI_2 download datasheet | AOZ1335DI_2 datasheet | AOZ1335DI_2 stock |
| buy AOZ1335DI_2 | Alpha and Omega Semiconductor, Inc. | Alpha and Omega Semiconductor, Inc. | Alpha & Omega Semiconductor AOZ1335DI_2 |
| | AOZ1335DI_2 | AOZ1335DI_2 | Alpha & Omega Semiconductor Inc. AOZ1335DI_2 |