







 
 














**IXD611S7**

	<p><b>IXYS</b></p> <p><b>Part Number:</b> <a href="#">IXD611S7</a></p> <p><b>Manufacturer:</b> <a href="#">IXYS Corporation</a></p> <p><b>Description:</b> IC DRVR HALF BRIDGE 600MA 14SOIC</p> <p><b>Data sheet:</b>  <a href="#">IXD611</a></p>	<p><b>RoHS Status:</b> Lead free / RoHS Compliant</p> <p><b>Ship From:</b> Hong Kong</p> <p><b>Shipment Way:</b> DHL/Fedex/TNT/UPS/EMS</p>
<p>Images are for reference only. See Product Specifications for product details. <b>Buy IXD611S7 with confidence from Component-World.HK, 1 Year Warranty</b></p>		
<a href="#" style="background-color: #007bff; color: white; padding: 5px 15px; border-radius: 3px;">Request For Quotation</a>		

PRODUCT PARAMETER			
<b>Part Number</b>	IXD611S7	<b>Manufacturer</b>	<a href="#">IXYS Corporation</a>
<b>Description</b>	IC DRVR HALF BRIDGE 600MA 14SOIC	<b>Lead Free Status / RoHS Status</b>	Lead free / RoHS Compliant
<b>Quantity Available</b>	4569 pcs	<b>Data sheet</b>	<a href="#">IXD611</a>
<b>Category</b>	<a href="#">Integrated Circuits (ICs)</a>	<b>Voltage - Supply</b>	10 V ~ 35 V
<b>Supplier Device Package</b>	14-SOIC	<b>Series</b>	-
<b>Rise / Fall Time (Typ)</b>	28ns, 18ns	<b>Packaging</b>	Bulk
<b>Package / Case</b>	14-SOIC (0.154", 3.90mm Width)	<b>Operating Temperature</b>	-40°C ~ 150°C (TJ)
<b>Number of Drivers</b>	2	<b>Mounting Type</b>	Surface Mount
<b>Moisture Sensitivity Level (MSL)</b>	1 (Unlimited)	<b>Logic Voltage - VIL, VIH</b>	2.4V, 2.7V
<b>Lead Free Status / RoHS Status</b>	Lead free / RoHS Compliant	<b>Input Type</b>	Non-Inverting
<b>High Side Voltage - Max (Bootstrap)</b>	600V	<b>Gate Type</b>	IGBT, N-Channel MOSFET
<b>Driven Configuration</b>	Half-Bridge	<b>Detailed Description</b>	Half-Bridge Gate Driver IC Non-Inverting 14-SOIC
<b>Current - Peak Output (Source, Sink)</b>	600mA, 600mA	<b>Channel Type</b>	Independent
<b>Base Part Number</b>	IX*611		

Component-World.com is a Reliable Stocking Distributor of Electronic Components. We specialize in all IXYS Corporation series electronic components. We have 4569 pieces of IXYS Corporation IXD611S7 in stock available now. Request a quote from electronics components distributor at Component-World.com, our sales team will contact you within 24 hours.  
RFQ Email: [info@Components-World.com](mailto:info@Components-World.com)

RELATED PRODUCTS			
	<p><b>Part#:</b> <a href="#">IXD5120N302NR-G</a></p> <p><b>Description:</b> IC VOLT DETECTOR 3.0V OD 24SSOT</p>	<p><b>Manufacturers:</b> <a href="#">Zilog</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD5120N152NR-G</a></p> <p><b>Description:</b> IC VOLT DETECTOR 1.5V OD 24SSOT</p>	<p><b>Manufacturers:</b> <a href="#">Zilog</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD5120C302NR-G</a></p> <p><b>Description:</b> IC VOLT DETECT 3.0V CMOS 24SSOT</p>	<p><b>Manufacturers:</b> <a href="#">Zilog</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD611P7</a></p> <p><b>Description:</b> IC DRVR HALF BRIDGE 600MA 14-PDI</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDD404SI</a></p> <p><b>Description:</b> IC MOSFET DRVR LS 4A DUAL 8SOIC</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDD408CI</a></p> <p><b>Description:</b> IC MOSFET DRVR LS 8A SGL 5TO-220</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD611S1</a></p> <p><b>Description:</b> IC DRVR HALF BRIDGE 600MA 8-SOIC</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD611P1</a></p> <p><b>Description:</b> IC DRVR HALF BRIDGE 600MA 8DIP</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD611S7T/R</a></p> <p><b>Description:</b> IC DRVR HALF BRIDGE 600MA 14SOIC</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDA20N120AS-TUBE</a></p> <p><b>Description:</b> IGBT 1200V 38A 200W TO263AB</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDA20N120AS</a></p> <p><b>Description:</b> IGBT 1200V 38A 200W TO263AB</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDD404SIA-16</a></p> <p><b>Description:</b> IC MOSFET DRVR DUAL 4A 16-SOIC</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDD404SI-16</a></p> <p><b>Description:</b> IC MOSFET DRVR LS 4A DUAL 16SOIC</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD5120C252NR-G</a></p> <p><b>Description:</b> IC VOLT DETECT 2.5V CMOS 24SSOT</p>	<p><b>Manufacturers:</b> <a href="#">Zilog</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD611S1T/R</a></p> <p><b>Description:</b> IC DRVR HALF BRIDGE 600MA 8-SOIC</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD5120N182NR-G</a></p> <p><b>Description:</b> IC VOLT DETECTOR 1.8V OD 24SSOT</p>	<p><b>Manufacturers:</b> <a href="#">Zilog</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDA20N120AS-TUB</a></p> <p><b>Description:</b> IGBT</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXD5120N252NR-G</a></p> <p><b>Description:</b> IC VOLT DETECTOR 2.5V OD 24SSOT</p>	<p><b>Manufacturers:</b> <a href="#">Zilog</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDD404PI</a></p> <p><b>Description:</b> IC MOSFET DRIVER LS 4A DUAL 8DIP</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>
	<p><b>Part#:</b> <a href="#">IXDD404SIA</a></p> <p><b>Description:</b> IC MOSFET DRVR DUAL 4A 8-SOIC</p>	<p><b>Manufacturers:</b> <a href="#">IXYS Corporation</a></p>	<a href="#" style="border: 1px solid #ccc; border-radius: 3px; padding: 2px 5px;">RFQ</a>

**Related keywords for IXD611S7**

IXYS Corporation IXD611S7	IXD611S7 distributor	IXD611S7 supplier	IXD611S7 price
IXD611S7 download datasheet	IXD611S7 datasheet	IXD611S7 stock	buy IXD611S7
IXYS Corporation IXD611S7	IXYS IXD611S7		