

LM358DR2



ON Semiconductor®

ON

Part Number:

LM358DR2

Manufacturer:

AMI Semiconductor / ON Semiconductor

Description:

IC OPAMP GP 1MHZ 8SOIC

Data sheet:

 [LM258, 358\(A\), 2904 \(A,V\), NCV2904 Datasheet](#)

RoHs Status:

Contains lead / RoHS non-compliant

Ship From:

Hong Kong

Shipment Way:

DHL/Fedex/TNT/UPS/EMS

Images are for reference only.
See Product Specifications for product details.
Buy LM358DR2 with confidence from Component-World.HK, 1 Year Warranty

Request For Quotation

PRODUCT PARAMETER			
Part Number	LM358DR2	Manufacturer	AMI Semiconductor / ON Semiconductor
Description	IC OPAMP GP 1MHZ 8SOIC	Lead Free Status / RoHS Status	Contains lead / RoHS non-compliant
Quantity Available	97573 pcs	Data sheet	LM258, 358(A), 2904 (A,V), NCV2904 Datasheet
Category	Integrated Circuits (ICs)	Voltage - Supply, Single/Dual (±)	3 V ~ 32 V, ±1.5 V ~ 16 V
Voltage - Input Offset	2mV	Supplier Device Package	8-SOIC
Slew Rate	0.6 V/μs	Series	-
Packaging	Cut Tape (CT)	Package / Case	8-SOIC (0.154", 3.90mm Width)
Output Type	-	Other Names	LM358DR2OSCT
Operating Temperature	0°C ~ 70°C	Number of Circuits	2
Mounting Type	Surface Mount	Moisture Sensitivity Level (MSL)	1 (Unlimited)
Lead Free Status / RoHS Status	Contains lead / RoHS non-compliant	Gain Bandwidth Product	1MHz
Detailed Description	General Purpose Amplifier 2 Circuit 8-SOIC	Current - Supply	1.5mA
Current - Output / Channel	40mA	Current - Input Bias	45nA
Base Part Number	LM358	Amplifier Type	General Purpose

Component-World.com is a Reliable Stocking Distributor of Electronic Components. We specialize in all AMI Semiconductor / ON Semiconductor series electronic components. We have 97573 pieces of AMI Semiconductor / ON Semiconductor LM358DR2 in stock available now. Request a quote from electronics components distributor at Component-World.com, our sales team will contact you within 24 hours.
RFQ Email: info@Components-World.com

RELATED PRODUCTS			
	Part#: LM358DGKR Description: IC OPAMP GP 700KHZ 8VSSOP	Manufacturers: N/A	RFQ
	Part#: LM358DMR2G Description: IC OPAMP GP 1MHZ MICRO8	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM358DG4 Description: IC OPAMP GP 700KHZ 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM358DE4 Description: IC OPAMP GP 700KHZ 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM358DMR2 Description: IC OPAMP GP 1MHZ MICRO8	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM358F-GE2 Description: GROUND SENSE OPERATIONAL AMPLIFI	Manufacturers: LAPIS Semiconductor	RFQ
	Part#: LM358DGKR Description: IC OPAMP GP 700KHZ 8MSOP	Manufacturers: LAPIS Semiconductor	RFQ
	Part#: LM358DT Description: IC OPAMP GP 1.1MHZ 8SO	Manufacturers: LAPIS Semiconductor	RFQ
	Part#: LM358DR Description: IC OPAMP GP 700KHZ 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM358DRG3 Description: IC OPAMP GP 700KHZ 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM358DR Description: IC OPAMP GP 700KHZ 8SOIC	Manufacturers: LAPIS Semiconductor	RFQ
	Part#: LM358DG Description: IC OPAMP GP 1MHZ 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM358FVJ-E2 Description: GROUND SENSE OPERATIONAL AMPLIFI	Manufacturers: LAPIS Semiconductor	RFQ
	Part#: LM358DT Description: IC OPAMP GP 1.1MHZ 8SO	Manufacturers: STMicroelectronics	RFQ
	Part#: LM358EDR2G Description: IC OPAMP DUAL LOW PWR 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM358DGKRG4 Description: IC OPAMP GP 700KHZ 8VSSOP	Manufacturers: N/A	RFQ
	Part#: LM358DR2G Description: IC OPAMP GP 1MHZ 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM358FVM-GTR Description: GROUND SENSE OPERATIONAL AMPLIFI	Manufacturers: LAPIS Semiconductor	RFQ
	Part#: LM358DRG4 Description: IC OPAMP GP 700KHZ 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM358DRE4 Description: IC OPAMP GP 700KHZ 8SOIC	Manufacturers: N/A	RFQ

Related keywords for LM358DR2

AMI Semiconductor / ON Semiconductor LM358DR2	LM358DR2 distributor	LM358DR2 supplier	LM358DR2 price
LM358DR2 download datasheet	LM358DR2 datasheet	LM358DR2 stock	buy LM358DR2
AMI Semiconductor / ON Semiconductor LM358DR2	ON Semiconductor LM358DR2	Aptina / ON Semiconductor LM358DR2	Catalyst Semiconductor / ON Semiconductor LM358DR2
PulseCore Semiconductor / ON Semiconductor LM358DR2	Sanyo Semiconductor / ON Semiconductor LM358DR2		