

LM385BD-1.2R2



ON Semiconductor®

Part Number: [LM385BD-1.2R2](#)

Manufacturer: [AMI Semiconductor / ON Semiconductor](#)

Description: IC VREF SHUNT 1.235V 8SOIC

Data sheet:  [LM285, LM385B](#)

RoHs Status: Contains lead / RoHS non-compliant


Ship From: Hong Kong

Shipment Way: DHL/Fedex/TNT/UPS/EMS

Images are for reference only.
See Product Specifications for product details.
Buy LM385BD-1.2R2 with confidence from Component-World.HK, 1 Year Warranty

Request For Quotation

PRODUCT PARAMETER			
Part Number	LM385BD-1.2R2	Manufacturer	AMI Semiconductor / ON Semiconductor
Description	IC VREF SHUNT 1.235V 8SOIC	Lead Free Status / RoHS Status	Contains lead / RoHS non-compliant
Quantity Available	110237 pcs	Data sheet	LM285, LM385B
Category	Integrated Circuits (ICs)	Voltage - Output (Min/Fixed)	1.235V
Voltage - Input	-	Tolerance	±1%
Temperature Coefficient	80ppm/°C Typical	Supplier Device Package	8-SOIC
Series	-	Reference Type	Shunt
Packaging	Tape & Reel (TR)	Package / Case	8-SOIC (0.154", 3.90mm Width)
Output Type	Fixed	Operating Temperature	0°C ~ 70°C (TA)
Noise - 10Hz to 10kHz	60µVrms	Noise - 0.1Hz to 10Hz	-
Mounting Type	Surface Mount	Moisture Sensitivity Level (MSL)	1 (Unlimited)
Lead Free Status / RoHS Status	Contains lead / RoHS non-compliant	Detailed Description	Shunt Voltage Reference IC ±1% 20mA 8-SOIC
Current - Supply	-	Current - Output	20mA
Current - Cathode	20µA	Base Part Number	LM385B
Component-World.com is a Reliable Stocking Distributor of Electronic Components. We specialize in all AMI Semiconductor / ON Semiconductor series electronic components. We have 110237 pieces of AMI Semiconductor / ON Semiconductor LM385BD-1.2R2 in stock available now. Request a quote from electronics components distributor at Component-World.com, our sales team will contact you within 24 hours. RFQ Email: info@Components-World.com			

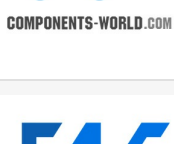RELATED PRODUCTS			
	Part#: LM385BD-2.5R2 Description: IC VREF SHUNT 2.5V 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM384N Description: IC AMP AUDIO PWR 5.5W MONO 14DIP	Manufacturers: N/A	RFQ
	Part#: LM384N/NOPB Description: IC AMP AUDIO PWR 5.5W MONO 14DIP	Manufacturers: N/A	RFQ
	Part#: LM385BDG4-1-2 Description: IC VREF SHUNT 1.235V 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM3824MMX-2.0 Description: IC CURRENT GAUGE PREC 8VSSOP	Manufacturers: N/A	RFQ
	Part#: LM385BD-1.2 Description: IC VREF SHUNT 1.235V 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM385BDE4-1-2 Description: IC VREF SHUNT 1.235V 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM385BD-1.2G Description: IC VREF SHUNT 1.235V 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM3824MM-2.0 Description: IC CURRENT GAUGE 3% 8VSSOP	Manufacturers: N/A	RFQ
	Part#: LM385BD-2.5R2G Description: IC VREF SHUNT 2.5V 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM385BD-2.5 Description: IC VREF SHUNT 2.5V 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM385-1.2-MWC Description: LM385-1.2-MWC	Manufacturers: N/A	RFQ
	Part#: LM385BD-1-2 Description: IC VREF SHUNT 1.235V 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM3824MMX-1.0 Description: IC CURRENT GAUGE PREC 8VSSOP	Manufacturers: N/A	RFQ
	Part#: LM385BD-2.5G Description: IC VREF SHUNT 2.5V 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM385BDE4-2-5 Description: IC VREF SHUNT 2.5V 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM385BDR-1-2 Description: IC VREF SHUNT 1.235V 8SOIC	Manufacturers: N/A	RFQ
	Part#: LM3824MM-1.0/NOPB Description: IC CURRENT GAUGE 3% 8VSSOP	Manufacturers: N/A	RFQ
	Part#: LM385BD-1.2R2G Description: IC VREF SHUNT 1.235V 8SOIC	Manufacturers: AMI Semiconductor / ON Semiconductor	RFQ
	Part#: LM385BD-2-5 Description: IC VREF SHUNT 2.5V 8SOIC	Manufacturers: N/A	RFQ

Related keywords for **LM385BD-1.2R2**

AMI Semiconductor / ON Semiconductor LM385BD-1.2R2	LM385BD-1.2R2 distributor	LM385BD-1.2R2 supplier	LM385BD-1.2R2 price
	LM385BD-1.2R2 download datasheet	LM385BD-1.2R2 datasheet	LM385BD-1.2R2 stock
buy LM385BD-1.2R2	AMI Semiconductor / ON Semiconductor LM385BD-1.2R2	ON Semiconductor LM385BD-1.2R2	Aptina / ON Semiconductor LM385BD-1.2R2
		Catalyst Semiconductor / ON Semiconductor LM385BD-1.2R2	PulseCore Semiconductor / ON Semiconductor LM385BD-1.2R2
Sanyo Semiconductor / ON Semiconductor LM385BD-1.2R2			

