

LT1228CS8#TRPBF





AHEAD OF WHAT'S POSSIBLE™

Part Number: [LT1228CS8#TRPBF](#)

Manufacturer: [ADI \(Analog Devices, Inc.\)](#)

Description: IC OPAMP CFA 100MHZ 8SO

Data sheet:  [Mac OS X Shortcuts](#)
 [LTspice Flyer](#)
 [LTspice IV Getting Started Guide](#)
 [LT1228 Datasheet](#)

RoHs Status: Lead free / RoHS Compliant



Ship From: Hong Kong

Shipment Way: DHL/Fedex/TNT/UPS/EMS

Images are for reference only.
See Product Specifications for product details.
Buy LT1228CS8#TRPBF with confidence from
Component-World.HK, 1 Year Warranty

Request For Quotation

PRODUCT PARAMETER			
Part Number	LT1228CS8#TRPBF	Manufacturer	ADI (Analog Devices, Inc.)
Description	IC OPAMP CFA 100MHZ 8SO	Lead Free Status / RoHS Status	Lead free / RoHS Compliant
Quantity Available	18141 pcs	Data sheet	Mac OS X Shortcuts LTspice Flyer LTspice IV Getting Started Guide LT1228 Datasheet
Category	Integrated Circuits (ICs)	Voltage - Supply, Single/Dual (±)	4 V ~ 36 V, ±2 V ~ 18 V
Voltage - Input Offset	3mV	Supplier Device Package	8-SO
Slew Rate	3500 V/μs	Series	-
Packaging	Cut Tape (CT)	Package / Case	8-SOIC (0.154", 3.90mm Width)
Output Type	-	Other Names	LT1228CS8#TRPBFCT
Operating Temperature	0°C ~ 70°C	Number of Circuits	1
Mounting Type	Surface Mount	Moisture Sensitivity Level (MSL)	1 (Unlimited)
Manufacturer Standard Lead Time	12 Weeks	Lead Free Status / RoHS Status	Lead free / RoHS Compliant
Detailed Description	Current Feedback Amplifier 1 Circuit 8-SO	Current - Supply	6mA
Current - Output / Channel	125mA	Current - Input Bias	10μA
Base Part Number	LT1228	Amplifier Type	Current Feedback
-3db Bandwidth	100MHz		
Component-World.com is a Reliable Stocking Distributor of Electronic Components. We specialize in all ADI (Analog Devices, Inc.) series electronic components. We have 18141 pieces of ADI (Analog Devices, Inc.) LT1228CS8#TRPBF in stock available now. Request a quote from electronics components distributor at Component-World.com, our sales team will contact you within 24 hours. RFQ Email: info@Components-World.com			

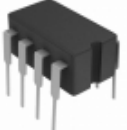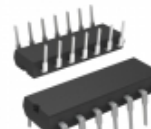RELATED PRODUCTS			
	Part#: LT1228IS8#TRPBF Description: IC OPAMP CFA 100MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1226CN8#PBF Description: IC OPAMP GP 1GHZ 8DIP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1227MJ8 Description: IC AMP CFA VIDEO 140MHZ Cerdip	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1226CS8#PBF Description: IC OPAMP GP 1GHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1229CN8#PBF Description: IC OPAMP CFA 100MHZ 8DIP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1230CN#PBF Description: IC OPAMP CFA 100MHZ 14DIP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1227CN8#PBF Description: IC VIDEO CURRNT FEEDBCK AMP 8DIP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1228CS8#PBF Description: IC OPAMP CFA 100MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1236ACN8-10#PBF Description: IC VREF SERIES/SHUNT 10V 8DIP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1225CS8#TRPBF Description: IC OPAMP GP 150MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1228IS8#PBF Description: IC OPAMP CFA 100MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1229CS8#PBF Description: IC OPAMP CFA 100MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1230CS#TRPBF Description: IC OPAMP CFA 100MHZ 14SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1228CN8#PBF Description: IC OPAMP CFA 100MHZ 8DIP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1229CS8#TRPBF Description: IC OPAMP CFA 100MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1230CS#PBF Description: IC OPAMP CFA 100MHZ 14SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1228IN8#PBF Description: IC OPAMP CFA 100MHZ 8DIP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1226CS8#TRPBF Description: IC OPAMP GP 1GHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1227CS8#PBF Description: IC VIDEO CURRNT FEEDBK AMP 8SOIC	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1227CS8#TRPBF Description: IC VIDEO CURRNT FEEDBK AMP 8SOIC	Manufacturers: ADI (Analog Devices, Inc.)	RFQ

Related keywords for LT1228CS8#TRPBF			
ADI (Analog Devices, Inc.) LT1228CS8#TRPBF	LT1228CS8#TRPBF distributor	LT1228CS8#TRPBF supplier	LT1228CS8#TRPBF price
LT1228CS8#TRPBF download datasheet	LT1228CS8#TRPBF datasheet	LT1228CS8#TRPBF stock	buy LT1228CS8#TRPBF
ADI (Analog Devices, Inc.) LT1228CS8#TRPBF	AD LT1228CS8#TRPBF	ADI (Analog Devices, Inc.) LT1228CS8#TRPBF	Analog Devices Inc. LT1228CS8#TRPBF
Analog Devices, Inc. LT1228CS8#TRPBF			

Reliable Stocking Distributor of Electronic Components © 2003-2021 Component-World.com All Rights Reserved.
E-mail: info@Components-World.com

