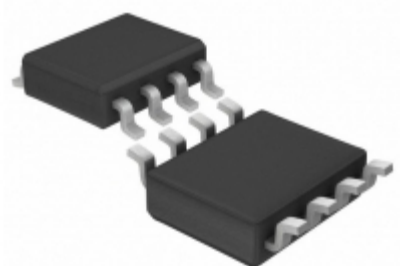


LT1810CS8#TRPBF





AHEAD OF WHAT'S POSSIBLE™

Part Number: [LT1810CS8#TRPBF](#)

Manufacturer: [ADI \(Analog Devices, Inc.\)](#)

Description: IC OPAMP GP 180MHZ RRO 8SO

Data sheet: [PDF Mac OS X Shortcuts](#)
[PDF LTspice Flyer](#)
[PDF LTspice IV Getting Started Guide](#)
[PDF LT1809, LT1810 Datasheet](#)

RoHs Status: Lead free / RoHS Compliant

Ship From: Hong Kong

Shipment Way: DHL/Fedex/TNT/UPS/EMS

Images are for reference only.
See Product Specifications for product details.
Buy **LT1810CS8#TRPBF** with confidence from
Component-World.HK, 1 Year Warranty

Request For Quotation

PRODUCT PARAMETER			
Part Number	LT1810CS8#TRPBF	Manufacturer	ADI (Analog Devices, Inc.)
Description	IC OPAMP GP 180MHZ RRO 8SO	Lead Free Status / RoHS Status	Lead free / RoHS Compliant
Quantity Available	28026 pcs	Data sheet	Mac OS X Shortcuts LTspice Flyer LTspice IV Getting Started Guide LT1809, LT1810 Datasheet
Category	Integrated Circuits (ICs)	Voltage - Supply, Single/Dual (±)	2.5 V ~ 12.6 V, ±1.25 V ~ 6.3 V
Voltage - Input Offset	800µV	Supplier Device Package	8-SO
Slew Rate	350 V/µs	Series	-
Packaging	Tape & Reel (TR)	Package / Case	8-SOIC (0.154", 3.90mm Width)
Output Type	Rail-to-Rail	Other Names	LT1810CS8#TRPBF-ND LT1810CS8#TRPBFTR
Operating Temperature	0°C ~ 70°C	Number of Circuits	2
Mounting Type	Surface Mount	Moisture Sensitivity Level (MSL)	1 (Unlimited)
Manufacturer Standard Lead Time	12 Weeks	Lead Free Status / RoHS Status	Lead free / RoHS Compliant
Gain Bandwidth Product	180MHz	Detailed Description	General Purpose Amplifier 2 Circuit Rail-to-Rail 8-SO
Current - Supply	15mA	Current - Output / Channel	85mA
Current - Input Bias	12.5µA	Base Part Number	LT1810
Amplifier Type	General Purpose	-3db Bandwidth	320MHz
Component-World.com is a Reliable Stocking Distributor of Electronic Components. We specialize in all ADI (Analog Devices, Inc.) series electronic components. We have 28026 pieces of ADI (Analog Devices, Inc.) LT1810CS8#TRPBF in stock available now. Request a quote from electronics components distributor at Component-World.com, our sales team will contact you within 24 hours. RFQ Email: info@Components-World.com			

RELATED PRODUCTS			
	Part#: LT1812CS6#TRPBF Description: IC OPAMP VFB 100MHZ TSOT23-6	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1812CS5#TRMPBF Description: IC OPAMP VFB 100MHZ TSOT23-5	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1809IS8#PBF Description: IC OPAMP GP 180MHZ RRO 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1810CMS8#TRPBF Description: IC OPAMP GP 180MHZ RRO 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1810IS8#PBF Description: IC OPAMP GP 180MHZ RRO 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1812CS8#TRPBF Description: IC OPAMP VFB 100MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1810IS8#TRPBF Description: IC OPAMP GP 180MHZ RRO 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1812CS5#TRPBF Description: IC OPAMP VFB 100MHZ TSOT23-5	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1809CS6#TRPBF Description: IC OPAMP GP 180MHZ RRO TSOT23-6	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1812CS8#PBF Description: IC OPAMP VFB 100MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1810IMS8#TRPBF Description: IC OPAMP GP 180MHZ RRO 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1809IS6#TRMPBF Description: IC OPAMP GP 180MHZ RRO TSOT23-6	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1810IMS8#PBF Description: IC OPAMP GP 180MHZ RRO 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1810CS8#PBF Description: IC OPAMP GP 180MHZ RRO 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1810CMS8#PBF Description: IC OPAMP GP 180MHZ RRO 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1812CS6#TRMPBF Description: IC OPAMP VFB 100MHZ TSOT23-6	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1809IS8#TRPBF Description: IC OPAMP GP 180MHZ RRO 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1809IS6#TRPBF Description: IC OPAMP GP 180MHZ RRO TSOT23-6	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1809CS8#PBF Description: IC OPAMP GP 180MHZ RRO 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1809CS8#TRPBF Description: IC OPAMP GP 180MHZ RRO 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ

Related keywords for LT1810CS8#TRPBF			
ADI (Analog Devices, Inc.) LT1810CS8#TRPBF	LT1810CS8#TRPBF distributor	LT1810CS8#TRPBF supplier	LT1810CS8#TRPBF price
LT1810CS8#TRPBF download datasheet	LT1810CS8#TRPBF datasheet	LT1810CS8#TRPBF stock	buy LT1810CS8#TRPBF
ADI (Analog Devices, Inc.) LT1810CS8#TRPBF	AD LT1810CS8#TRPBF	ADI (Analog Devices, Inc.) LT1810CS8#TRPBF	Analog Devices Inc. LT1810CS8#TRPBF
Analog Devices, Inc. LT1810CS8#TRPBF			

Reliable Stocking Distributor of Electronic Components © 2003-2021 Component-World.com All Rights Reserved.
E-mail: info@Components-World.com

