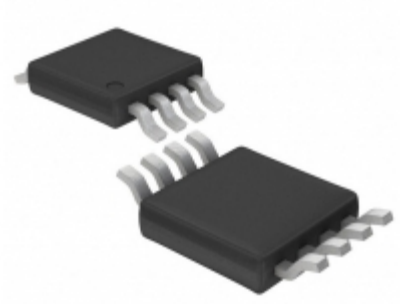


LT1999MPMS8-20#TRPBF





AHEAD OF WHAT'S POSSIBLE™

Part Number: [LT1999MPMS8-20#TRPBF](#)

Manufacturer: [ADI \(Analog Devices, Inc.\)](#)

Description: IC OPAMP CURR SENSE 2MHZ 8MSOP

Data sheet:  [LT1999-10,20,50 Datasheet](#)
 [Mac OS X Shortcuts](#)
 [LTspice Flyer](#)
 [LTspice IV Getting Started Guide](#)

RoHs Status: Lead free / RoHS Compliant


Ship From: Hong Kong

Shipment Way: DHL/Fedex/TNT/UPS/EMS

Images are for reference only.
See Product Specifications for product details.
Buy LT1999MPMS8-20#TRPBF with confidence from
Component-World.HK, 1 Year Warranty

Request For Quotation

PRODUCT PARAMETER			
Part Number	LT1999MPMS8-20#TRPBF	Manufacturer	ADI (Analog Devices, Inc.)
Description	IC OPAMP CURR SENSE 2MHZ 8MSOP	Lead Free Status / RoHS Status	Lead free / RoHS Compliant
Quantity Available	17515 pcs	Data sheet	LT1999-10,20,50 Datasheet Mac OS X Shortcuts LTspice Flyer LTspice IV Getting Started Guide
Category	Integrated Circuits (ICs)	Voltage - Supply, Single/Dual (±)	4.5 V ~ 5.5 V
Voltage - Input Offset	500µV	Supplier Device Package	8-MSOP
Slew Rate	3 V/µs	Series	-
Packaging	Tape & Reel (TR)	Package / Case	8-TSSOP, 8-MSOP (0.118", 3.00mm Width)
Output Type	-	Operating Temperature	-55°C ~ 150°C
Number of Circuits	1	Mounting Type	Surface Mount
Moisture Sensitivity Level (MSL)	1 (Unlimited)	Manufacturer Standard Lead Time	12 Weeks
Lead Free Status / RoHS Status	Lead free / RoHS Compliant	Detailed Description	Current Sense Amplifier 1 Circuit 8-MSOP
Current - Supply	5.8mA	Current - Input Bias	137.5µA
Base Part Number	LT1999	Amplifier Type	Current Sense
-3db Bandwidth	2MHz		
Component-World.com is a Reliable Stocking Distributor of Electronic Components. We specialize in all ADI (Analog Devices, Inc.) series electronic components. We have 17515 pieces of ADI (Analog Devices, Inc.) LT1999MPMS8-20#TRPBF in stock available now. Request a quote from electronics components distributor at Component-World.com, our sales team will contact you within 24 hours. RFQ Email: info@Components-World.com			

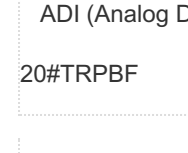RELATED PRODUCTS			
	Part#: LT1999MPMS8-20F#PBF Description: IC OP AMP CUR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-50#PBF Description: IC OPAMP CURR SENSE 1.2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPS8-20#TRPBF Description: IC OPAMP CURR SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999IS8-50#PBF Description: IC OPAMP CURR SENSE 1.2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPS8-10#TRPBF Description: IC OPAMP CURR SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-50F#TRPBF Description: IC OP AMP CUR SENSE 1.2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPS8-20#PBF Description: IC OPAMP CURR SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-10#PBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-50#TRPBF Description: IC OPAMP CURR SENSE 1.2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-20#PBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-10F#PBF Description: IC OP AMP CUR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-50F#PBF Description: IC OP AMP CUR SENSE 1.2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-10#TRPBF Description: IC OPAMP CURR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-10F#TRPBF Description: IC OP AMP CUR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPS8-10#PBF Description: IC OPAMP CURR SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999MPMS8-20F#TRPBF Description: IC OP AMP CUR SENSE 2MHZ 8MSOP	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999IS8-10#TRPBF Description: IC OPAMP CURRENT SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999IS8-50#TRPBF Description: IC OPAMP CURR SENSE 1.2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999IS8-20#PBF Description: IC OPAMP CURRENT SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ
	Part#: LT1999IS8-20#TRPBF Description: IC OPAMP CURRENT SENSE 2MHZ 8SO	Manufacturers: ADI (Analog Devices, Inc.)	RFQ

Related keywords for **LT1999MPMS8-20#TRPBF**

ADI (Analog Devices, Inc.) LT1999MPMS8-20#TRPBF	LT1999MPMS8-20#TRPBF distributor	LT1999MPMS8-20#TRPBF supplier	LT1999MPMS8-20#TRPBF price
	LT1999MPMS8-20#TRPBF download datasheet	LT1999MPMS8-20#TRPBF datasheet	LT1999MPMS8-20#TRPBF stock
buy LT1999MPMS8-20#TRPBF	ADI (Analog Devices, Inc.) LT1999MPMS8-20#TRPBF	AD LT1999MPMS8-20#TRPBF	ADI (Analog Devices, Inc.) LT1999MPMS8-20#TRPBF
Analog Devices Inc. LT1999MPMS8-20#TRPBF	Analog Devices, Inc. LT1999MPMS8-20#TRPBF		

Reliable Stocking Distributor of Electronic Components © 2003-2021 Component-World.com All Rights Reserved.
E-mail: info@Components-World.com

